 


Lecture 3: Complementary Metal Oxide Semiconductor (CMOS)





Outline


- **CMOS Inverter Operating Principle**
 - Operating in logical high, low and transitions
- **CMOS Inverter Voltage Transfer Characteristic (VTC)**
 - Five operating regions
 - VTC Construction
- **CMOS Inverter Reliability and Design Rules**
 - Switching Threshold
 - Noise Margin 噪声容忍门限

Review: Switch Model of MOSFET

NMOS Transistor

 
 


$Y=Z$ if $X=1$

 


$Y \neq Z$ if $X=0$

PMOS Transistor

  


$Y \neq Z$ if $X=1$

 


$Y=Z$ if $X=0$

Review: I - V Curve of MOSFET

 

$$I_D(sat) = \frac{\mu_n C_{ox}}{2} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2$$

Long-Channel MOSFET
Pinch-Off Saturation

 

$$I_{DSAT} = v_{sat} \cdot C_{ox} \cdot W \cdot [V_{GS} - V_T - V_{DSAT}]$$

Short-Channel MOSFET
Velocity Saturation

Review: MOSFET Unified Model

$$V_{GT} = V_{GS} - V_T$$

◆ Active region ($V_{GT} \geq 0$) Lin, Sat, V-Sat

$$I_{DS} = \mu_n C_{ox} \cdot \frac{W}{L} \cdot (V_{GT} \cdot V_{\min} - \frac{V_{\min}^2}{2}) \cdot (1 + \lambda V_{DS})$$


$$V_{\min} = \min (V_{DS}, V_{GT}, V_{DSAT})$$




Lin Sat V-Sat

The CMOS Inverter


symbol

 


schematic

 

layout

 


CMOS Inverter Operational Principle

 

$$V_{in} = 0$$

$V_{GSn} = V_{in} = 0 \rightarrow \text{NMOS OFF}$

$|V_{GSp}| = V_{DD} - V_{in} > |V_{Tp}| \rightarrow \text{PMOS ON}$

 


□ The output is connected to V_{DD} through a low-impedance path.

□ The equivalent circuit is an RC circuit.

□ In steady state, $V_{out} = V_{DD}$, $V_{DSp} = 0$, NMOS OFF, PMOS in deep linear region, no static current.


CMOS Inverter Operational Principle

 

$$V_{in} = V_{DD}$$

$$V_{GSn} = V_{DD} > V_{Tn} \rightarrow \text{NMOS ON}$$
 
$$V_{GSp} = V_{DD} - V_{DD} = 0 \rightarrow \text{PMOS OFF}$$




□ The output is connected to GND through a low-impedance path.

□ The equivalent circuit is an RC circuit.

□ In steady state, $V_{out} = 0$, $V_{DSn} = 0$, PMOS OFF, NMOS in deep linear region, no static current.


CMOS Inverter Operational Principle

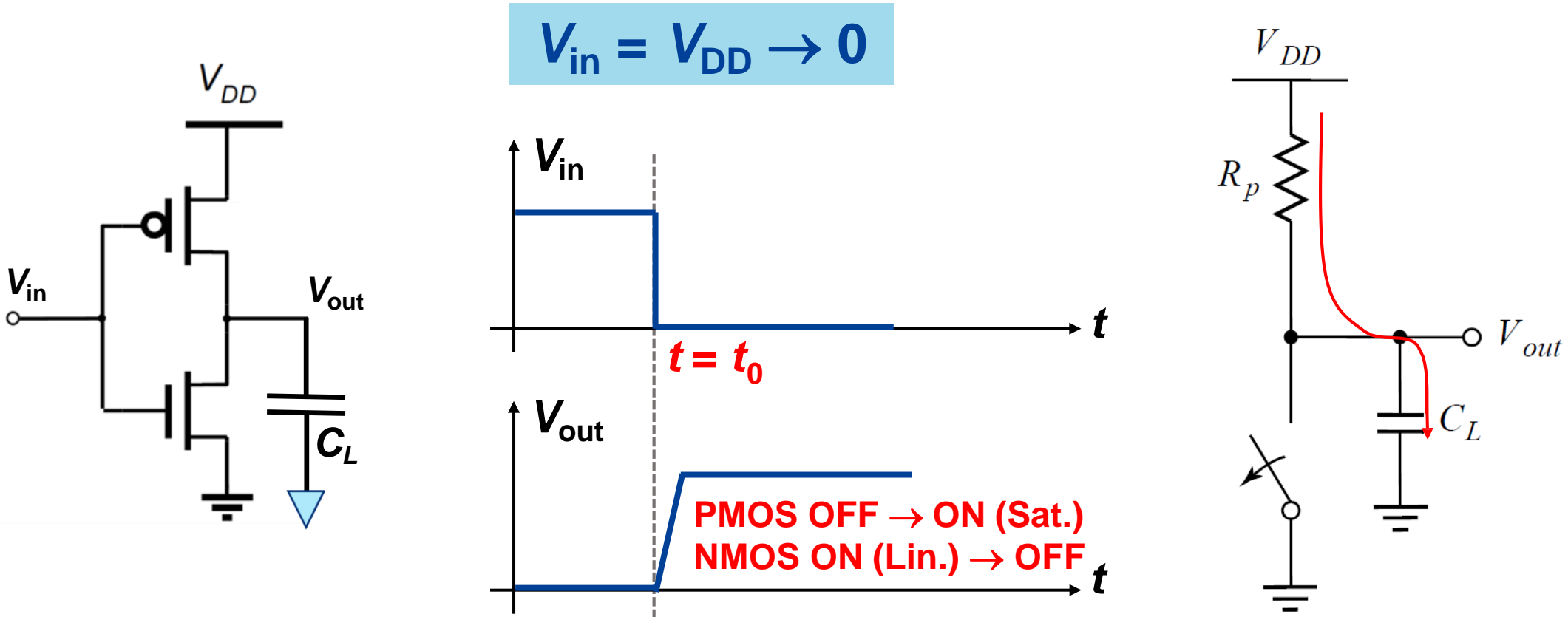

□ The V_{DD} charges the output through PMOS \rightarrow Pull-Up Process.

□ Finally, $V_{out} = 0 \rightarrow V_{DD}$.



CMOS Inverter Operational Principle

 

□ The output **discharges** through NMOS to GND \rightarrow **Pull-Down Process.**

□ Finally, $V_{out} = V_{DD} \rightarrow 0$.

CMOS Inverter Operational Principle

  

- The Inversion function is realized → CMOS Inverter.
- Rather than directly connect output, input controls the on/off of MOSFET and charge/discharge of capacitance

Ideal Static CMOS Properties

- Full rail-to-rail swing.
 - $V_{OL} = 0$, $V_{OH} = V_{DD}$
- Logic levels independent on transistor size.
 - “Ratio-less” logic
- Low output impedance ($k\Omega$ range).
- High input impedance ($\sim\infty$).
- No direct-path current in steady state.
 - No static power dissipation