 


Lecture 4: CMOS Inverter


Physical Characteristics



Outline

- **CMOS Inverter Equivalent Resistance and Capacitance**
 - Resistance vs. V_{DD}
 - Capacitance of Logic Circuit
- **CMOS Inverter Propagation Delay**
 - Delay vs. Resistance & Capacitance
 - Miller Theorem and C_{GD}
- **CMOS Inverter Power Consumption**
 - Static & Dynamic power
 - Switching Power Consumption
 - Short-circuit Power Consumption

Review: Equivalent Resistance

 



Method 1: Integration

$$R_{on} = \frac{1}{-V_{DD}/2} \int_{V_{DD}}^{V_{DD}/2} \frac{V}{I_{DSAT} \cdot (1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD}\right)$$

Method 2: Averaging

$$R_{on} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT} \cdot (1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT} \cdot (1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD}\right)$$



Review: Capacitance of MOSFET

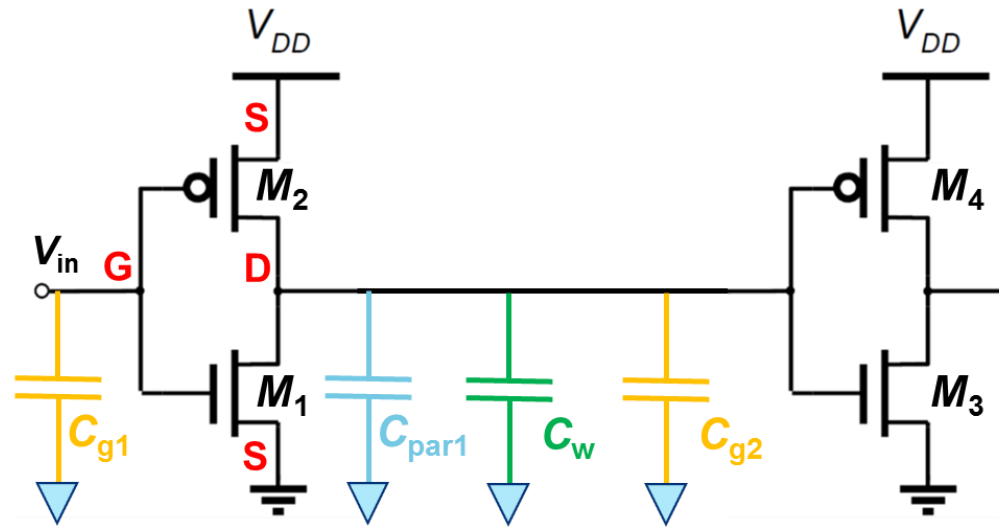 

- Gate Capacitance C_{GC} – parallel capacitance.
- Parasitic Capacitance C_{SB} and C_{DB} – p-n junction diffusion capacitance.
- The capacitance counts **ONLY** when the voltage across it changes during the **PUN** and/or **PDN** process.

CMOS Inverter Delay Definitions


$$t_p = (t_{pHL} + t_{pLH}) / 2$$

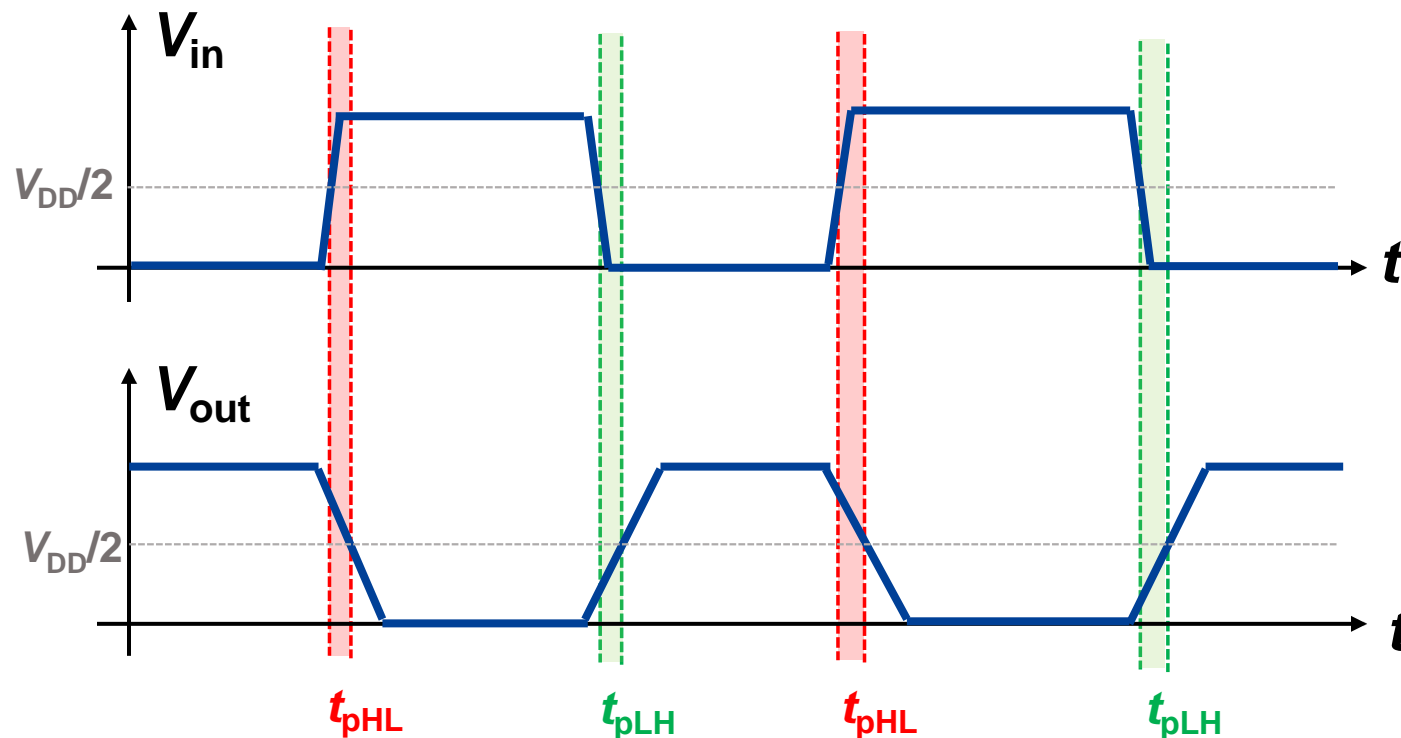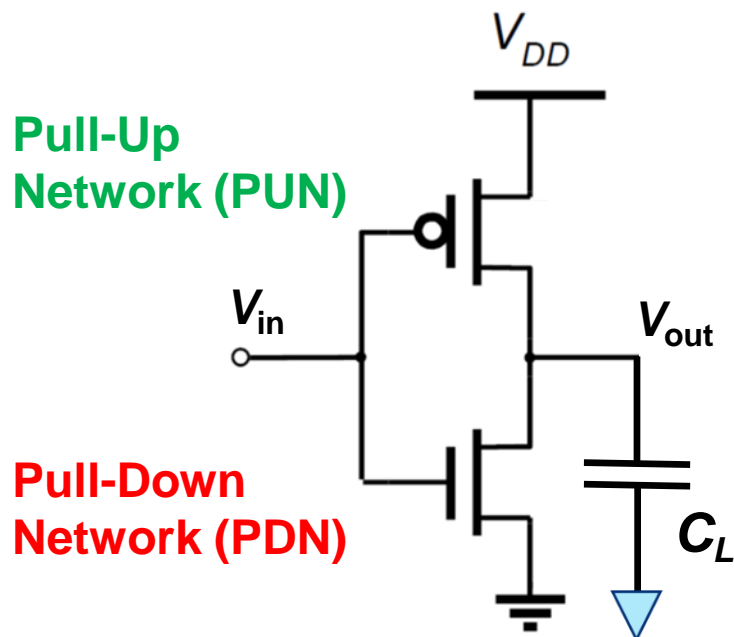

- Propagation time is the charge/discharge time of capacitance.
- During PDN functioning, C_L discharges, t_{pHL} relates to time difference of $V_{in} = V_{DD}/2 \rightarrow V_{out} = V_{DD}/2$.
- During PUN functioning, C_L charges, t_{pLH} relates to time difference of $V_{in} = V_{DD}/2 \rightarrow V_{out} = V_{DD}/2$.

Inverter Equivalent Circuit

 □ A first-order RC network: Step Response



Kirchhoff's Current Law

$$\frac{V_{in} - V_{out}}{R} = C_L \cdot \frac{dV_{out}}{dt}$$

□ The general solution of linear first-order differential equation $\frac{dy}{dx} + P(x)y = Q(x)$ is:

$$y = e^{-\int P(x)dx} \left(\int Q(x)e^{\int P(x)dx} dx + C \right)$$

$$V_{out}(t=0) = V_0$$

$$V_{out}(t=\infty) = V_\infty$$

$$V_{out}(t) = V_\infty + (V_0 - V_\infty) \cdot e^{-t/\tau}, \tau = RC$$


□ For PDN: $V_0 = V_{DD}$ & $V_\infty = 0$

$$V_{out}(t) = V_{DD} e^{-t/\tau_n}$$

□ For PUN: $V_0 = 0$ & $V_\infty = V_{DD}$


$$V_{out}(t) = V_{DD} (1 - e^{-t/\tau_p})$$

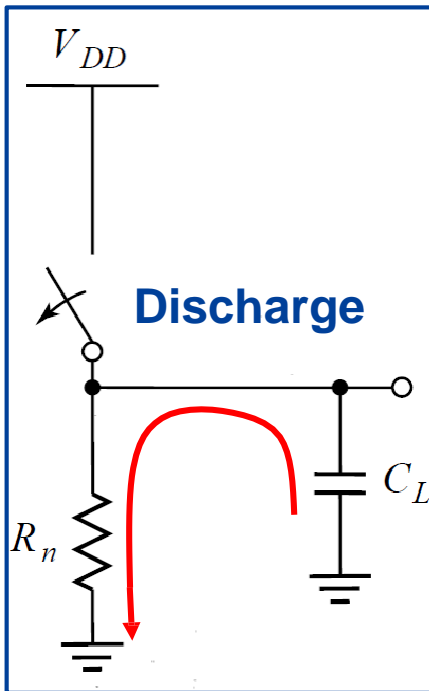PDN
 $V_{out} = V_{DD} \rightarrow V_{DD}/2$



$$\tau_n = R_n \cdot C_L$$

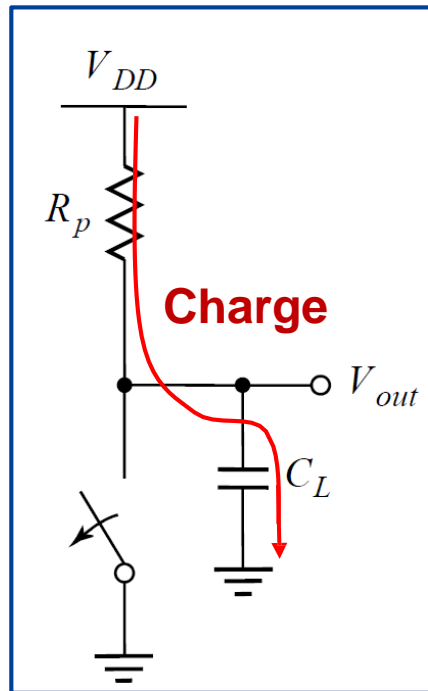PUN
 $V_{out} = V_{DD}/2 \rightarrow V_{DD}$



$$\tau_p = R_p \cdot C_L$$

$$V_{out}(t) = e^{-\int \frac{1}{RC} dt} \left(c_0 + \int \frac{V_{in}}{RC} e^{\int \frac{1}{RC} dt} dt \right)$$

$$= e^{-\frac{t}{RC}} \left[c_0 + \int \frac{V_{in}}{RC} e^{\frac{t}{RC}} dt \right]$$

$$= e^{-\frac{t}{RC}} \left[c_0 + V_{in} e^{\frac{t}{RC}} \right]$$

$$= V_{in} + c_0 e^{-\frac{t}{RC}}$$

$$\begin{cases} t=0 \text{ 时, } V_{out}(0) = V_{in} + c_0 = V_0 \\ t=\infty \text{ 时, } V_{out}(\infty) = V_{in} = V_{\infty} \end{cases}$$

 \Rightarrow

$$c_0 = V_0 - V_{\infty}$$


$$V_{in} = V_{\infty}$$

$$\Rightarrow V_{out}(t) = V_{\infty} + (V_0 - V_{\infty}) e^{-\frac{t}{RC}}$$

Inverter Propagation Delay

PDN
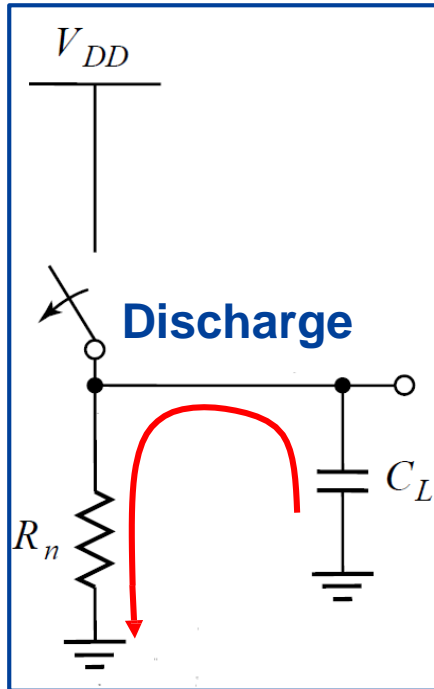
$$V_{out} = V_{DD} \rightarrow V_{DD}/2$$



□ A first-order RC discharge network

$$V_{out}(t) = V_{DD} e^{-t/\tau_n}, \quad \tau_n = R_n \cdot C_L$$

□ At $t = t_{pHL}$

$$V_{out}(t_{pHL}) = V_{DD} e^{-t_{pHL}/\tau_n} = V_{DD} / 2$$




$$t_{pHL} = \tau_n \ln \frac{V_{DD}}{V_{DD}/2} = \tau_n \ln 2 = 0.69 R_n \cdot C_L$$

□ Similarly, for PUN

$$V_{out}(t) = V_{DD} (1 - e^{-t/\tau_p}), \quad \tau_p = R_p \cdot C_L$$

$$t_{pLH} = \tau_p \ln 2 = 0.69 R_p \cdot C_L$$

Inverter Propagation Delay

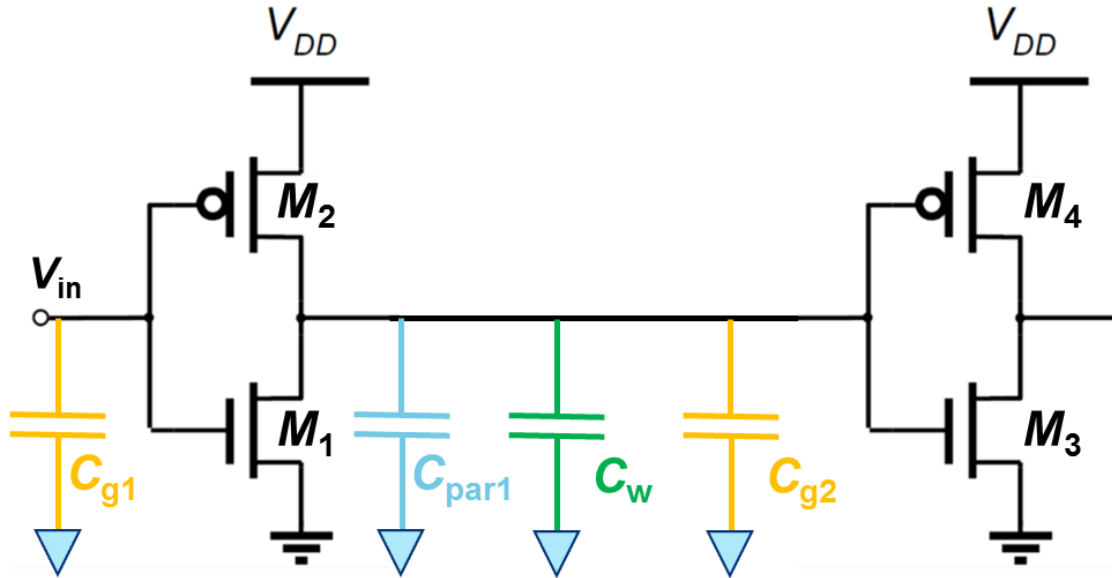


Goal: To optimize the propagation delay

- Modifying supply voltage V_{DD} -- equivalent resistance
- Sizing PMOS/NMOS ratio -- Switching Threshold


$$t_p = (t_{pHL} + t_{pLH}) / 2 = 0.69 R \cdot C_L = 0.69 \left(\frac{R_n + R_p}{2} \right) \cdot (C_{par1} + C_{g2} + C_w)$$

Inverter Delay as a Function of V_{DD}

Equivalent R_{on} vs. V_{DD}



 


$$t_p \propto R_{on}$$

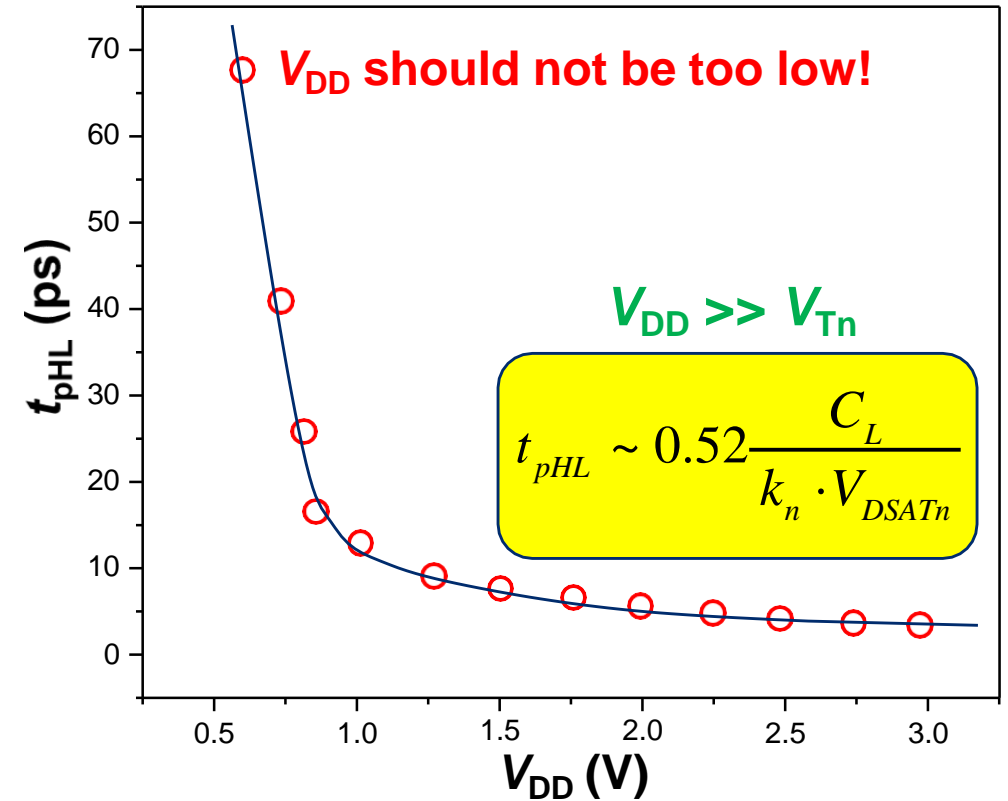

Inverter Delay vs. PMOS/NMOS Size Ratio

   
$$\beta = \frac{W_p}{L_p} / \frac{W_n}{L_n} = \frac{W_p}{W_n} \quad (L_n = L_p = L_0)$$



- Larger β (wider PMOS) means stronger PUN strength in terms of smaller R_p , higher V_M , and shorter t_{pLH} .
- We will choose $\beta = 2$ in this course as **standard inverter** for **optimized t_p** with **almost equivalent NMOS/PMOS strength and resistance**.

Propagation Delay vs. Inverter Sizing

Standard INV.

 

Neglect C_w and C_{GD}

Standard INV.

$$t_{p1} = t_{p,int} + t_{p,ext} = 0.69 \cdot [R_0 \cdot C_{par} + R_0 \cdot C_{g2}]$$

Increase the first INV. size by S


$$R_0 \rightarrow R_0/S$$

$$C_{par} \rightarrow C_{par} \cdot S, C_{g1} \rightarrow C_{g1} \cdot S$$

$$t_{p1} = t_{p,int} + t_{p,ext} = 0.69 R_0 \cdot C_{par1} + 0.69 \frac{R_0}{S} \cdot C_{g2}$$


Size Independent

Reduce with Size

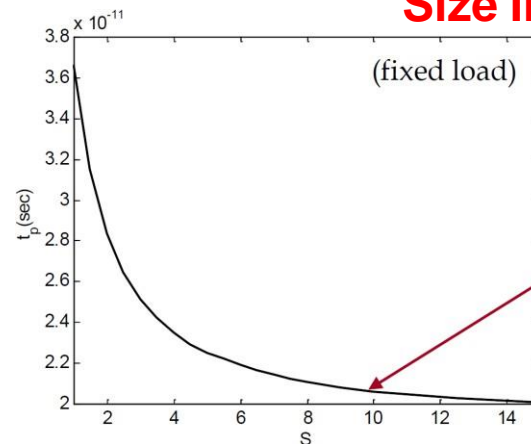


Self-loading effect:
Intrinsic capacitance dominates

The Effect of C_{GD}

 

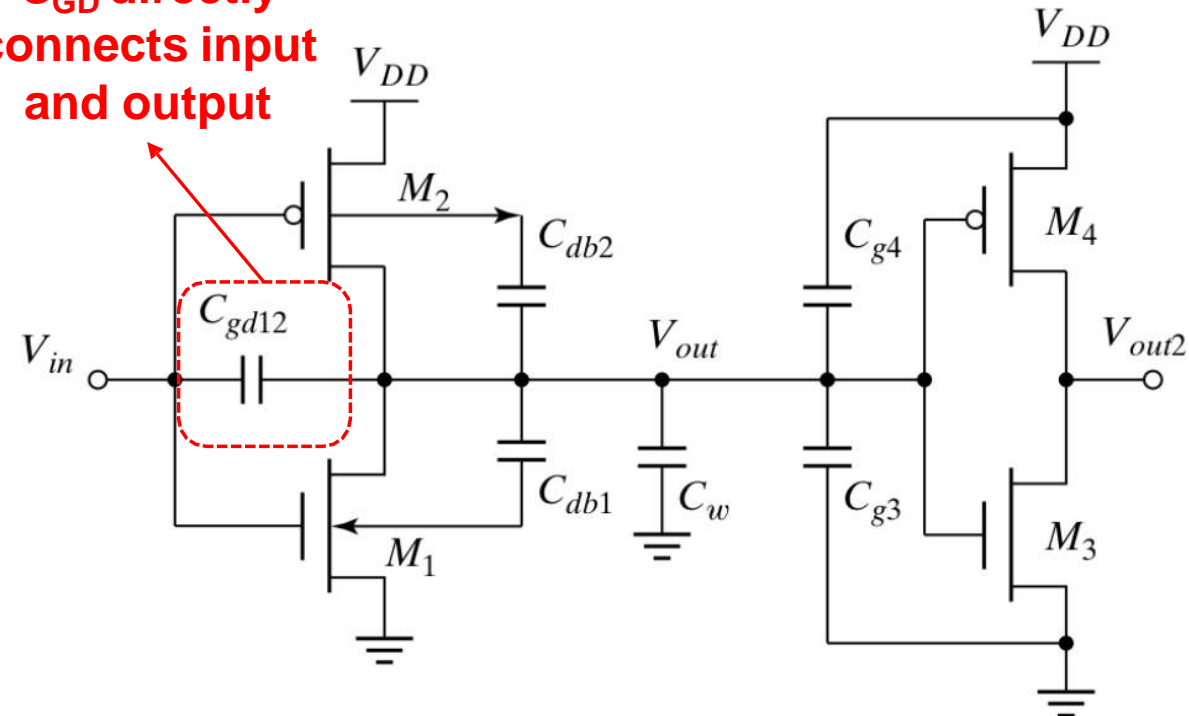
C_{GD} directly connects input and output



□ When V_{in} changes abruptly, the nature of C_{GD} ensures relative stable voltage drop across it at that moment.

Miller Theorem

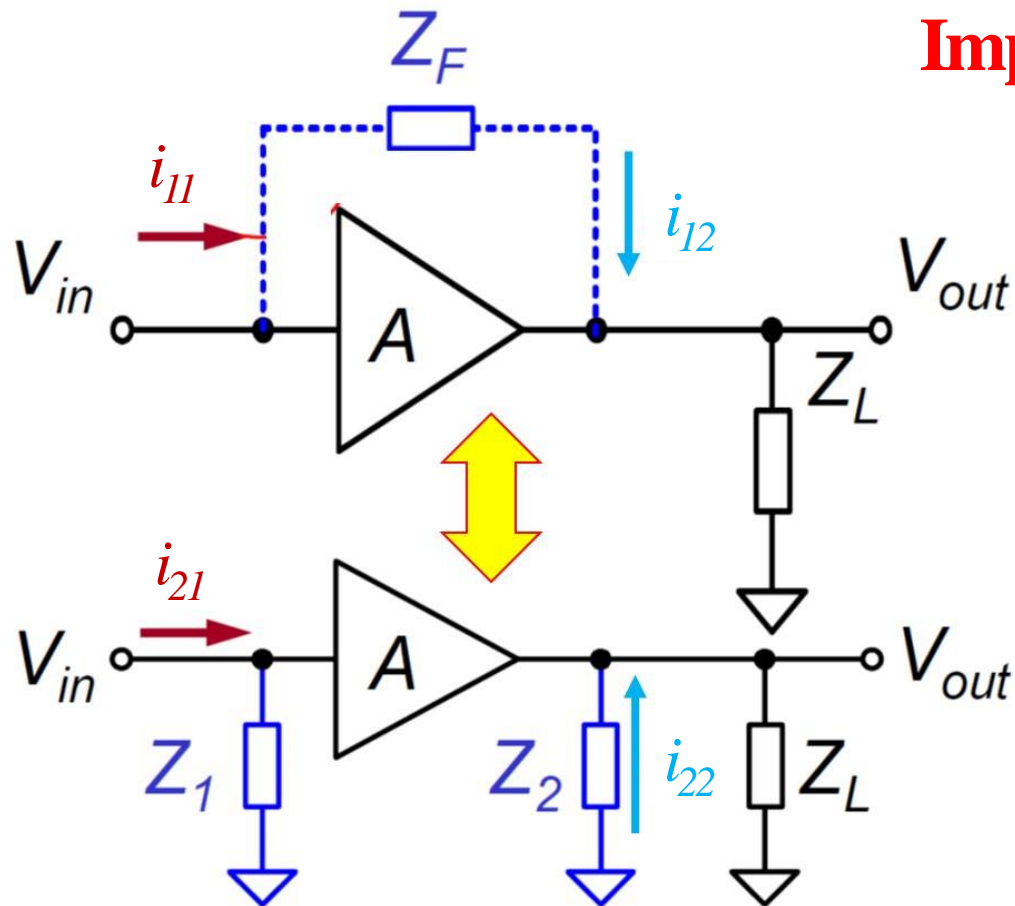- In an amplifier circuit, if the impedance is connected in between the input & output nodes, then connected impedance can be changed to two separated impedances near input & output respectively, and $Z_1 = Z/(1-A)$, $Z_2 = Z/(1-1/A)$.



Impedance -> resistance / inductance / capacitance

$$i_{11} = V_{in} \cdot \frac{1-A}{Z_F}, \quad i_{12} = i_{11}$$


Equivalent circuit: $i_{11} = i_{21}$
 $i_{12} = i_{22}$

$$i_{21} = V_{in} / Z_1$$

$$i_{22} = -AV_{in} / Z_2$$


$$Z_1 = \frac{Z_F}{1-A}, \quad Z_2 = \frac{Z_F}{1-1/A}$$

Miller Theorem and CMOS Inverter

 

$$Z_1 = \frac{Z_F}{1 - A}, \quad Z_2 = \frac{Z_F}{1 - 1/A} \quad \rightarrow \quad Z_1 = \frac{Z_F}{2}, \quad Z_2 = \frac{Z_F}{2} \quad \xrightarrow{Z=1/\omega C} \quad C_1 = C_2 = 2C_{GD}$$

Miller Theorem and CMOS Inverter

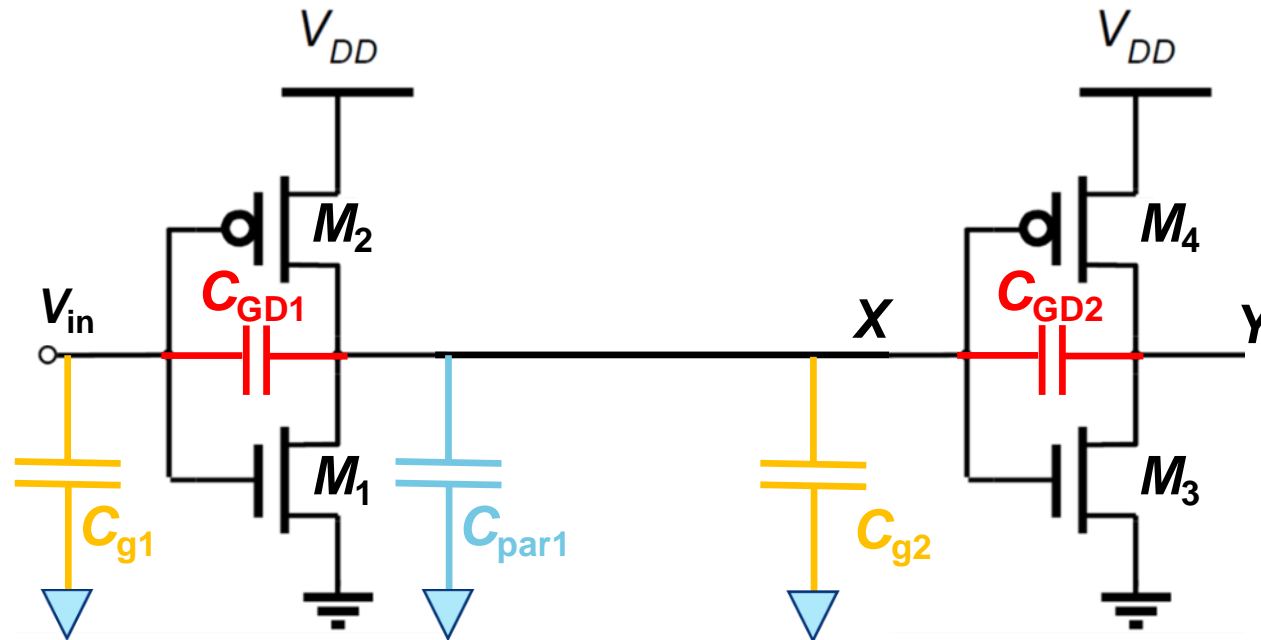

- C_{GD1} will contribute to t_{p1} by adding $2C_{GD1}$ to the output.
- Yet C_{GD2} will NOT affect t_{p1} due to the **relatively constant voltage difference between X and Y** during the process.