 




Lecture 3: Complementary Metal Oxide Semiconductor (CMOS)



Outline

- **CMOS Inverter Operating Principle**
 - Operating in logical high, low and transitions
- **CMOS Inverter Voltage Transfer Characteristic (VTC)**
 - Five operating regions
 - VTC Construction
- **CMOS Inverter Reliability and Design Rules**
 - Switching Threshold
 - Noise Margin 噪声容忍门限

Review: Static CMOS VTC

 
 


Noise in Digital ICs

❑ **Noise** – unwanted variations of voltages and currents at the logic nodes.


❑ **Digital system** is one where:

  - Analog signals are quantized to discrete values
- All the elements (gates) can somehow reject noise
- For sufficiently “small” noise, the system acts as if it was noise-free




- For large noise, the logic state may be changed!

Switching Threshold of Inverter

 

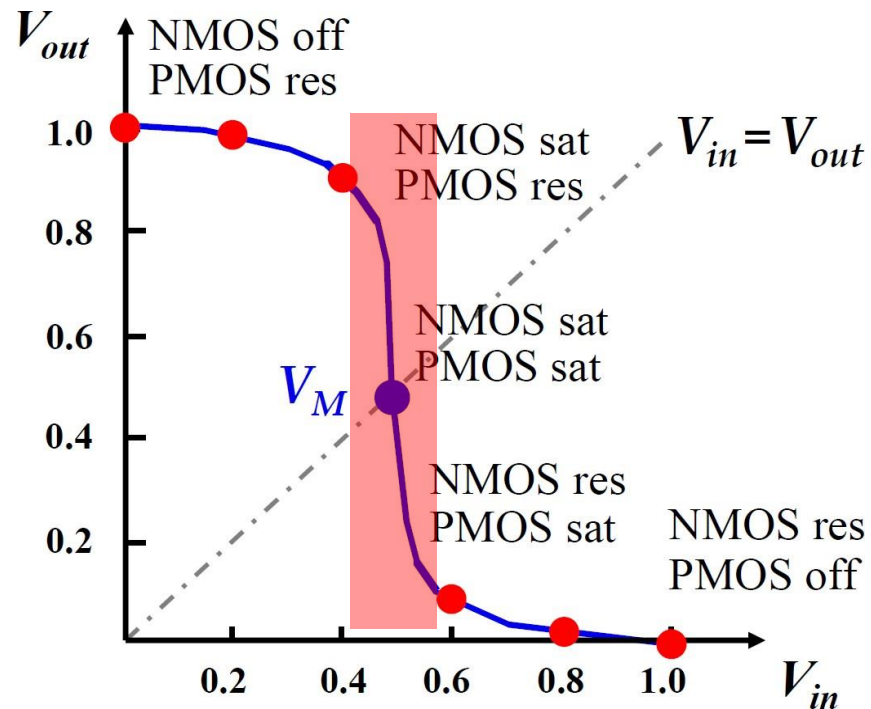- The switching threshold compares the relative driving strengths between the NMOS and PMOS
- At switching threshold: $V_{in} = V_{out} = V_M$
- $V_{DS} = V_{GS} \rightarrow$ Both PMOS & NMOS are saturated



Switching Threshold Calculation

□ Apply Kirchhoff's Current Law & Velocity-Sat I - V Model (neglecting CLM)

$$\underbrace{k_n \cdot V_{DSATn} \cdot \left(V_M - V_{Tn} - \frac{V_{DSATn}}{2} \right)}_{\substack{k_n = \mu_n C_{ox} \frac{W_n}{L} \\ I_{Dn}}} + \underbrace{k_p \cdot V_{DSATp} \cdot \left(V_M - V_{DD} - V_{Tp} - \frac{V_{DSATp}}{2} \right)}_{\substack{k_p = \mu_p C_{ox} \frac{W_p}{L} \\ -I_{Dp}}} = 0$$

□ Solving for V_M


$$V_M = \frac{(V_{Tn} + \frac{V_{DSATn}}{2}) + r(V_{DD} + V_{Tp} + \frac{V_{DSATp}}{2})}{1 + r}$$

$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$$


Key: $v_{sat} = \mu \cdot V_{DSAT} / L$

□ For large V_{DD}


$$V_M \approx \frac{r V_{DD}}{1 + r}$$

 

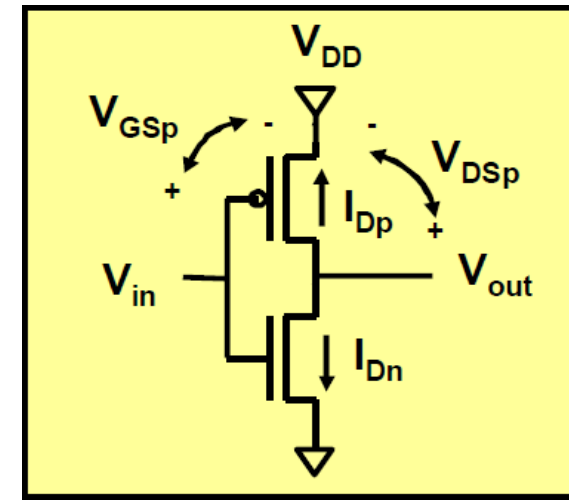V_M can be controlled by transistor size!





Real Case Switching Threshold Variation

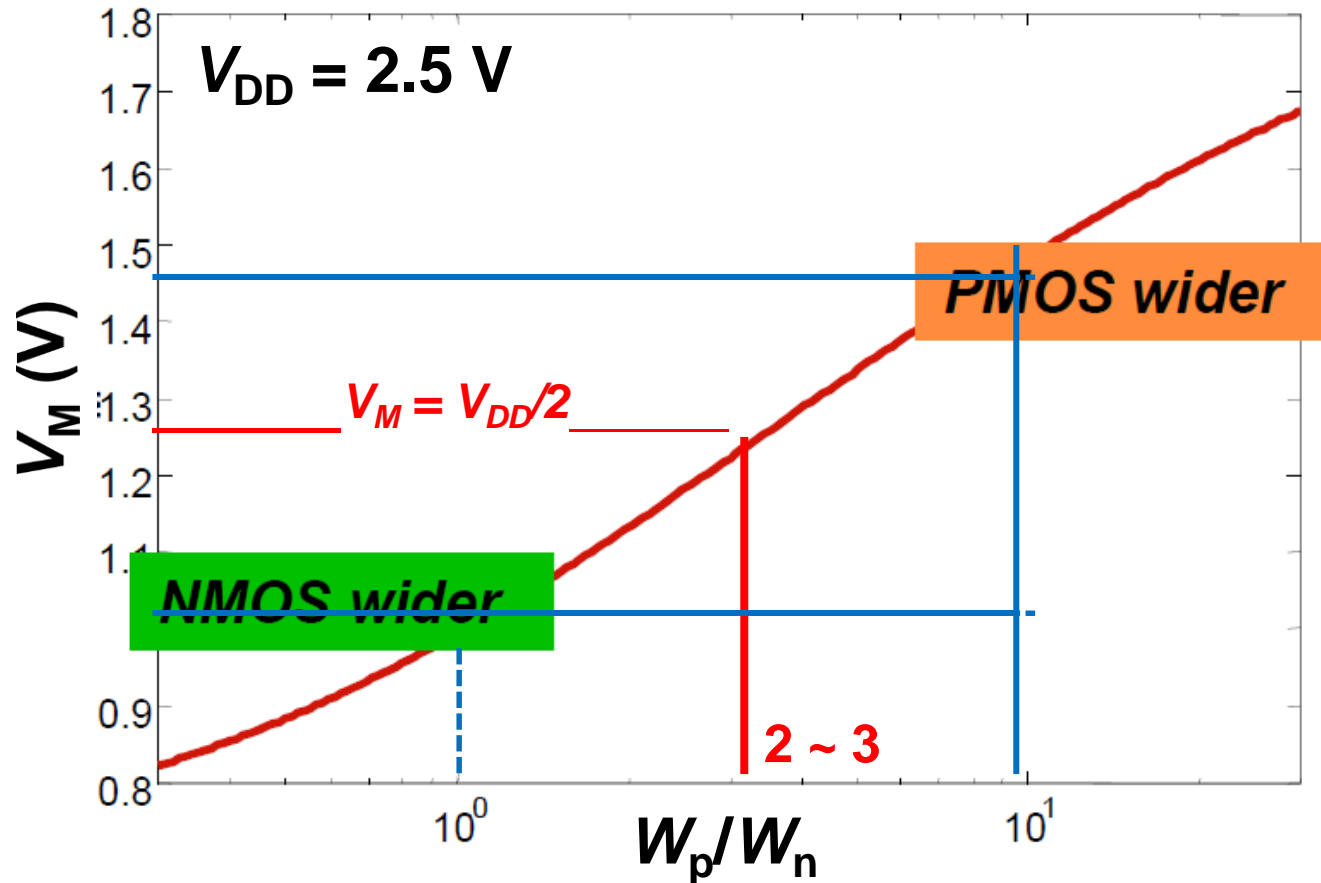

□ Increasing the width of PMOS moves V_M towards V_{DD} whereas increasing the width of NMOS moves V_M towards GND

□ To make $V_M = V_{DD}/2$, we need to choose a wider PMOS.

Impact of Process Variations

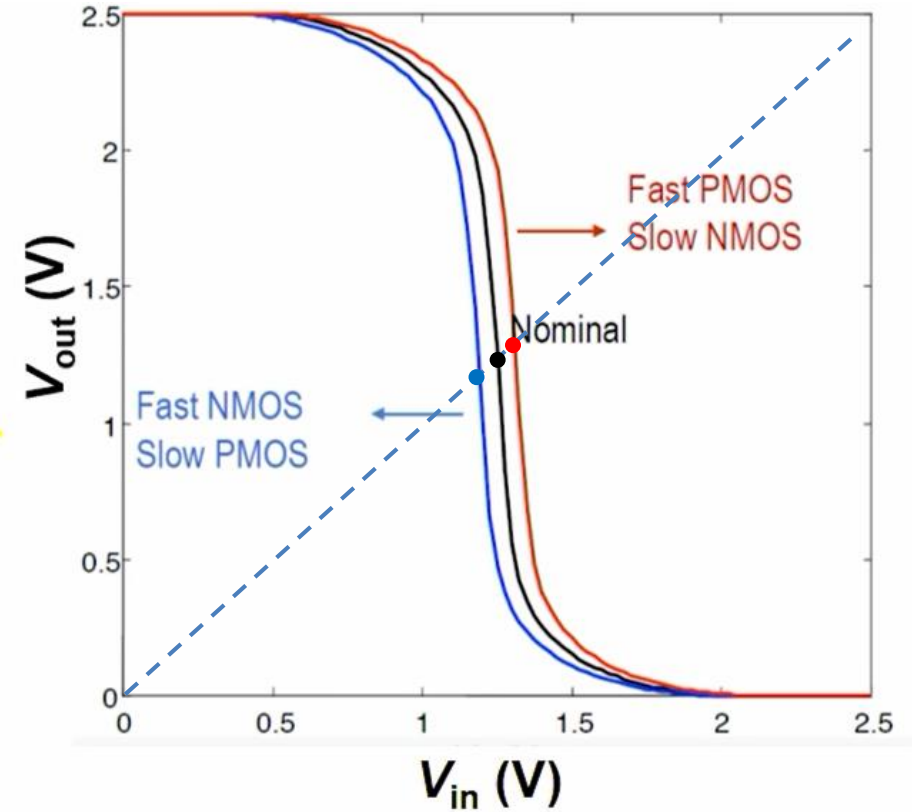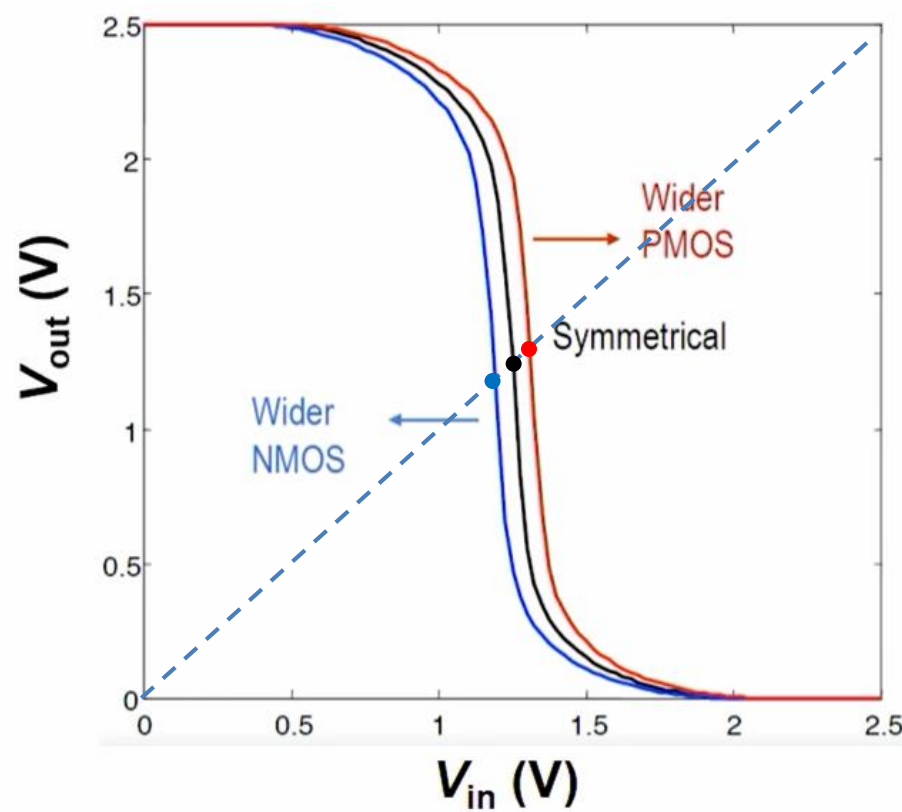


**r decreases
Strong NMOS**


$$r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}} = \frac{v_{satp} W_p}{v_{satn} W_n}$$

**r increases
Strong PMOS**

Impact of Supply Voltage V_{DD}

 

Large Supply Voltage

 

Small Supply Voltage

Noise Rejection

□ To see if a gate rejects noise





- Look at its DC voltage transfer characteristic (VTC)
- See what happens when input is **not** exactly 1 or 0

□ Ideal digital gate:


- Noise needs to be larger than $V_{DD}/2$ to have any effect on gate output





DC Operation – More Realistic VTC

    

Noise Margin

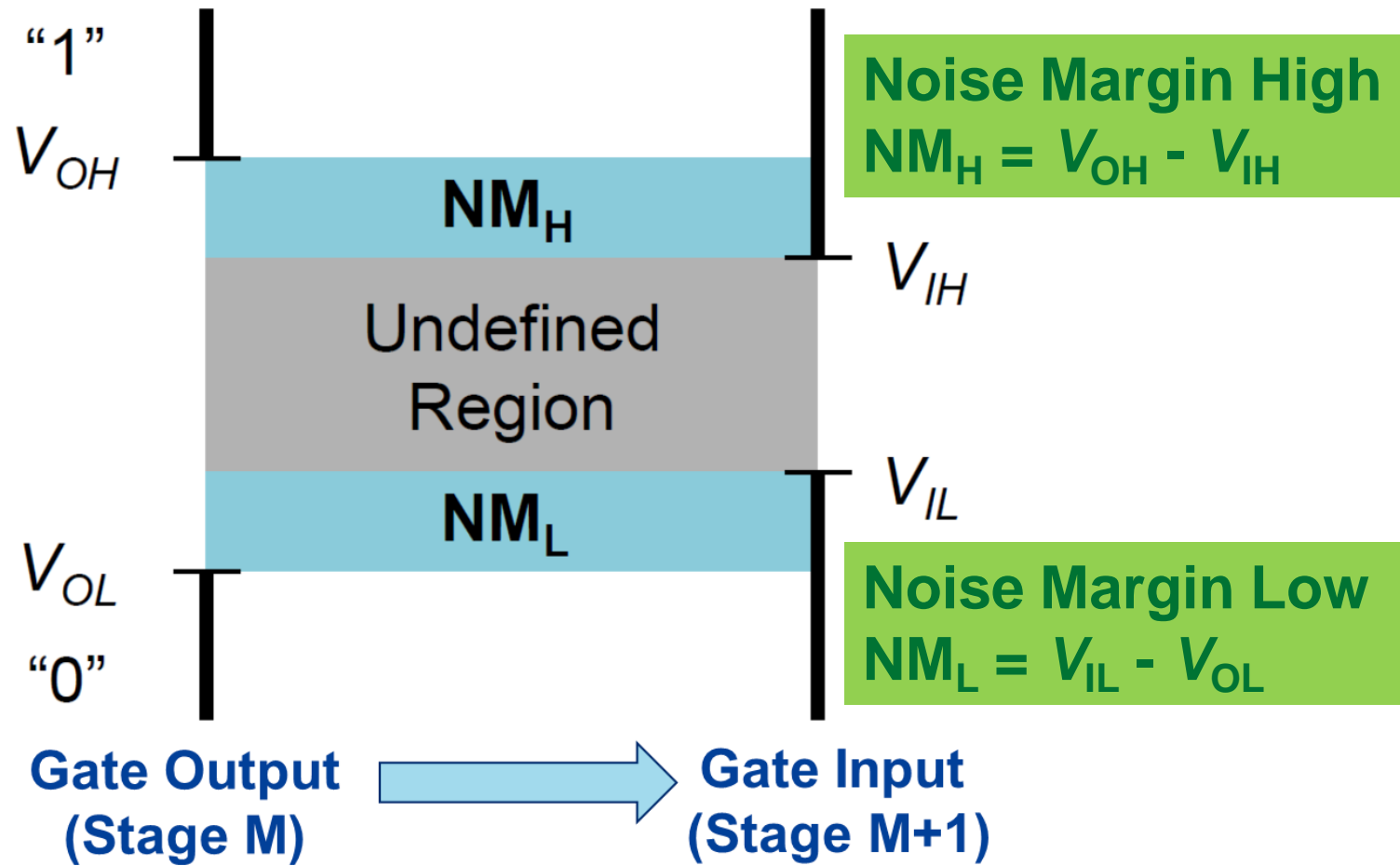


Ideal Case vs. Real Case

  


Noise Rejection of Inverter Chain

□ A chain of inverters

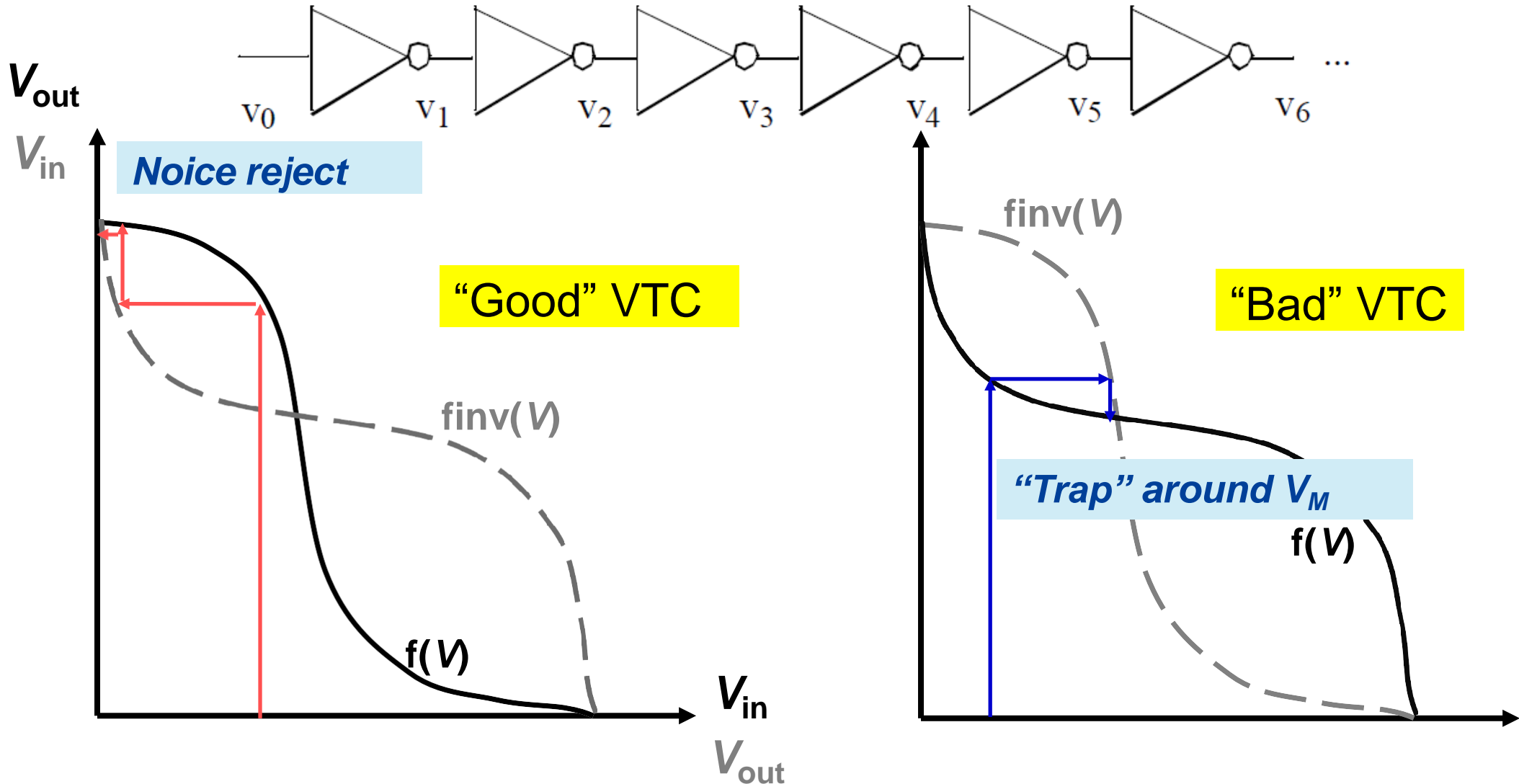

Summary of Static CMOS Inverter

 

- Static CMOS inverter is the simplest logic gate for digital integrated circuit design.
- VTC of static CMOS inverter is obtained by analyzing the operation regions of NMOS & PMOS.
- Region 1 and region 4 are ideal operation regions.
- static CMOS inverter serves as the building block for static CMOS logic gates.