 


Lecture 4: CMOS Inverter

Physical Characteristics




Outline


- **CMOS Inverter Equivalent Resistance and Capacitance**
 - Resistance vs. V_{DD}
 - Capacitance of Logic Circuit
- **CMOS Inverter Propagation Delay**
 - Delay vs. Resistance & Capacitance
 - Miller Theorem and C_{GD}
- **CMOS Inverter Power Consumption**
 - Static & Dynamic power
 - Switching Power Consumption
 - Short-circuit Power Consumption

The CMOS Inverter


symbol

 


schematic

 


Voltage Transfer Characteristic (VTC)

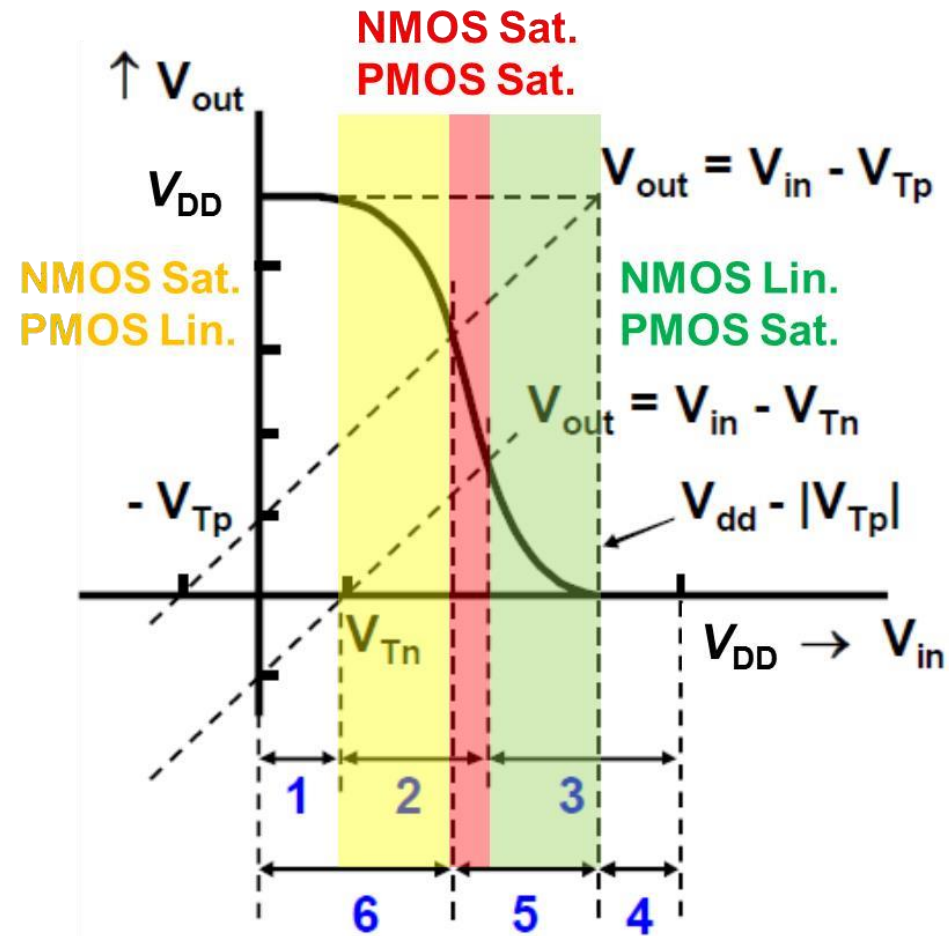


CMOS Inverter Operational Principle

 

$$V_{in} = V_{DD} \rightarrow 0$$

 


$$V_{in} = 0 \rightarrow V_{DD}$$

 

- The equivalent circuit of CMOS inverter is a first-order RC network.
- Need to know R and C first.


Review: I - V Characteristic of MOSFET

 

$$I_{DS} = \mu_n C_{ox} \cdot \frac{W}{L} \cdot \left(V_{GT} \cdot V_{\min} - \frac{V_{\min}^2}{2} \right) \cdot (1 + \lambda V_{DS})$$

take derivation of V_{DS}
 
$$1/R_{on} = \mu_n C_{ox} \cdot \frac{W}{L} \cdot \left(V_{GT} \cdot V_{\min} - \frac{V_{\min}^2}{2} \right) \lambda$$





$$V_{\min} = \min(V_{DS}, V_{GT}, V_{DSAT})$$

Lin Sat V-Sat

Equivalent Resistance of Inverter

$$I_{DS} = \mu_n C_{ox} \cdot \frac{W}{L} \cdot (V_{GT} \cdot V_{\min} - \frac{V_{\min}^2}{2}) \cdot (1 + \lambda V_{DS})$$
  
$$V_{in} = V_{DD}, V_{out} = V_{DD} \rightarrow V_{DD}/2$$



□ NMOS in Vel. Sat. $V_{\min} = V_{DSAT}$

$$I_{DSAT} = \mu_n C_{ox} \cdot \frac{W}{L} \cdot \left(V_{GT} \cdot V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

$$I_{DS}(V_{DS}) = I_{DSAT} \cdot (1 + \lambda V_{DS})$$




□ Calculating equivalent resistance

$$R(V_{DS}) = \frac{V_{DS}}{I_{DSAT} \cdot (1 + \lambda V_{DS})}$$

Computing NMOS Equivalent Resistance

$$R(V_{DS}) = \frac{V_{DS}}{I_{DSAT} \cdot (1 + \lambda V_{DS})}$$

 

Method 1: Integration

$$R_{on} = \frac{1}{-V_{DD}/2} \int_{V_{DD}}^{V_{DD}/2} \frac{V}{I_{DSAT} \cdot (1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD}\right)$$


Method 2: Averaging

$$R_{on} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT} \cdot (1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT} \cdot (1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD}\right)$$

R_{on} vs. V_{DD} – Simulation Results

- R_{on} increases linearly (yet with smooth slope) as V_{DD} reduces from large value.
- Tend to scale with $1/V_{DD}$ and increase dramatically as V_{DD} approaches V_T

Cadence Simulation Result

 

$$R_{on} = \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD} \right)$$

$$I_{DSAT} = \mu_n C_{ox} \cdot \frac{W}{L} \cdot \left((V_{GS} - V_T) \cdot V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

$(V_{GS} = V_G - V_{DD})$

□ V_{DD} is large

$$V_{DSAT}, V_G \ll V_{DD}$$



$$I_{DSAT} \propto V_{DD}$$

□ V_{DD} is small

$$V_{DSAT}, V_G \sim V_{DD}$$


$$I_{DSAT} \propto V_{DD}^2$$

Capacitance of the MOSFET

  


- Gate Capacitance C_{GC} – parallel capacitance.
- Parasitic Capacitance C_{SB} and C_{DB} – p-n junction diffusion capacitance.
- The capacitance counts only when the voltage across it changes during the PUN and/or PDN process.


Gate Capacitance

 

Cut-Off

 


Linear/Resistive

 

Saturation


Operation Region	C_{GCB}	C_{GCS}	C_{GCD}	C_{GC}
Cut-Off	$C_{ox} WL_{eff}$	0	0	$C_{ox} WL_{eff}$
Linear	0	$C_{ox} WL_{eff}/2$	$C_{ox} WL_{eff}/2$	$C_{ox} WL_{eff}$
Saturation	0	$(2/3)C_{ox} WL_{eff}$	0	$(2/3)C_{ox} WL_{eff}$

Diffusion Capacitance

 

$$\begin{aligned}
 C_{diff} &= C_{bottom} + C_{sw} \\
 &= C_j \cdot AREA + C_{jsw} \cdot \overset{\text{周长}}{PERIMETER} \\
 &= C_j \cdot L_s W + C_{jsw} \cdot (2L_s + W)
 \end{aligned}$$

Capacitance in Logic Circuits

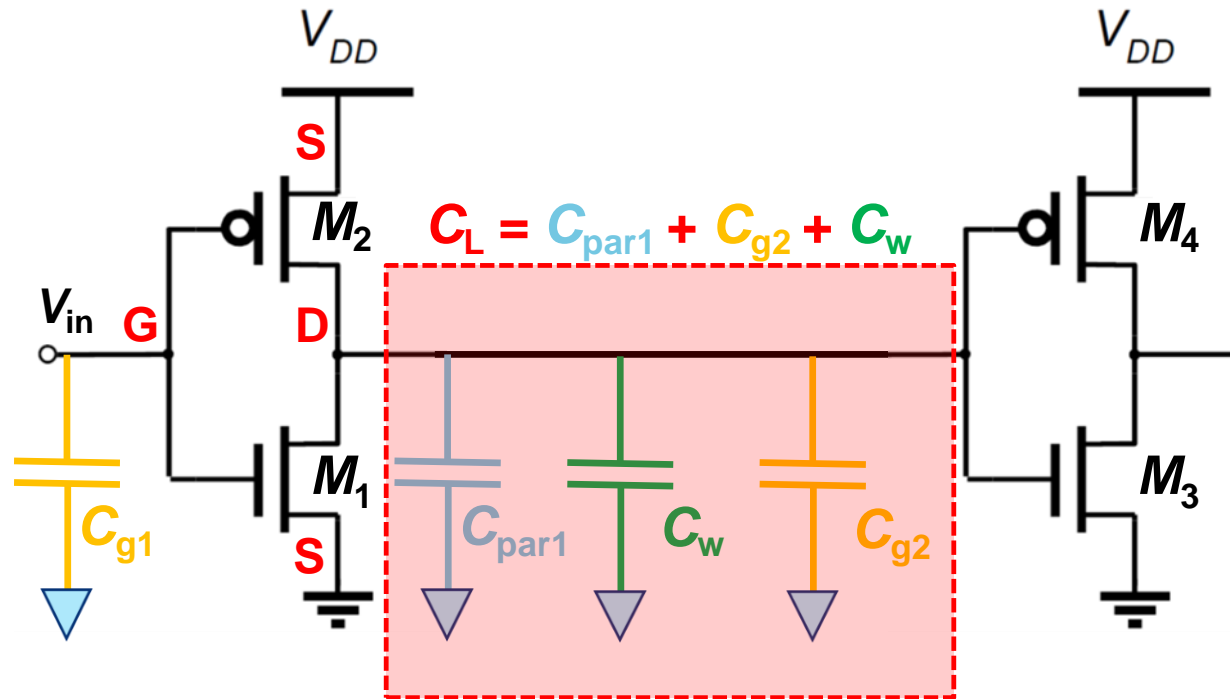

- C_{g1} – C_{GS} of M_1 and M_2 .
- C_{g2} – C_{GS} of M_3 and M_4 .
- C_{par1} – C_{DB} of M_1 and M_2 .
- C_w – parasitic cap. of wire.

◆ The body terminal is always connected to GND (NMOS) or V_{DD} (PMOS).