 


# Lecture 4: CMOS Inverter

## Physical Characteristics



# Outline

- **CMOS Inverter Equivalent Resistance and Capacitance**
  - Resistance vs.  $V_{DD}$
  - Capacitance of Logic Circuit
- **CMOS Inverter Propagation Delay**
  - Delay vs. Resistance & Capacitance
  - Miller Theorem and  $C_{GD}$
- **CMOS Inverter Power Consumption**
  - Static & Dynamic power
  - Switching Power Consumption
  - Short-circuit Power Consumption

# Tsunami of Data Era has Come!

- Over 2.5 billion computers in the world
  - 1 PW ( $10^{15}$  W) of power dissipation
  - Equivalent to 160 nuclear plants!
  - 'Tsunami of data' could consume 1/5 of global electricity by 2025!



Google Data Center



Facebook Data Center @ Sweden

# The Power in CMOS Inverter

## Dynamic power

### □ Switching power

- ◆ Charge/discharge capacitor

### □ Short-circuit power



- ◆ Both NMOS and PMOS ON during transition

### □ Gate / Junction Leakage power

- ◆ Gate / Drain to Body
- ◆ Relatively small

 
 
### □ Sub-threshold leakage power

- ◆  $I_{DS} > 0$  when  $V_{GS} < V_T$
- ◆  $I_{DS}$  increases as  $V_T$  decreases



## Static power

# Charging/discharging Consumption

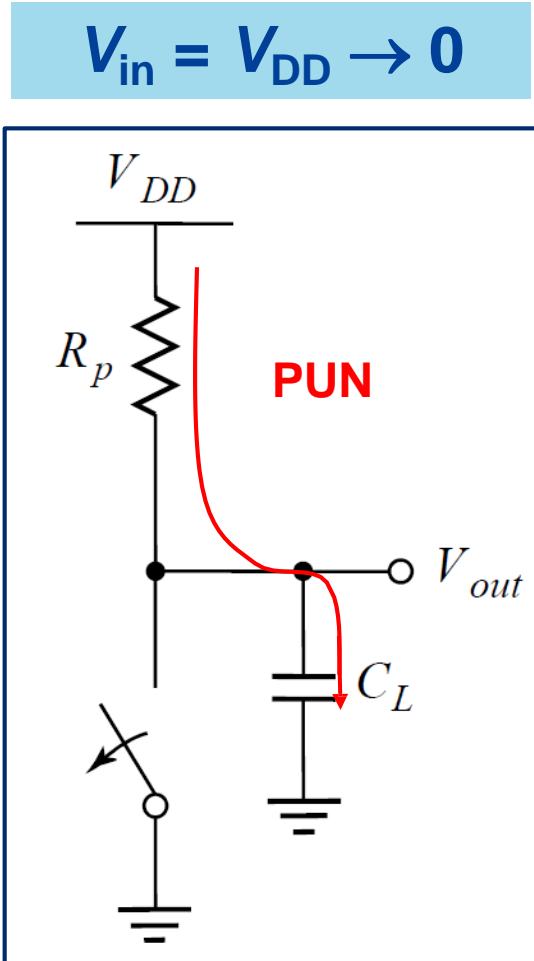 

$$E_{0 \rightarrow 1} = \int_{t=0}^{\infty} V_{DD} \cdot I_{Dp} \cdot dt$$

$$I_{Dp} = C_L \cdot \frac{dV_{out}}{dt}$$

□ CMOS Inverter  $V_{OH} = V_{DD}$ ,  $V_{OL} = 0$


$$E_{0 \rightarrow 1} = C_L \cdot V_{DD} \cdot \int_{V_{OL}}^{V_{OH}} dV_{out} = C_L \cdot V_{DD} \cdot (V_{OH} - V_{OL})$$

$$= C_L \cdot V_{DD}^2$$

Dynamic energy dissipation is  
NOT a function of transistor  
resistance or size!

# Charging/discharging Consumption

$$V_{in} = V_{DD} \rightarrow 0$$

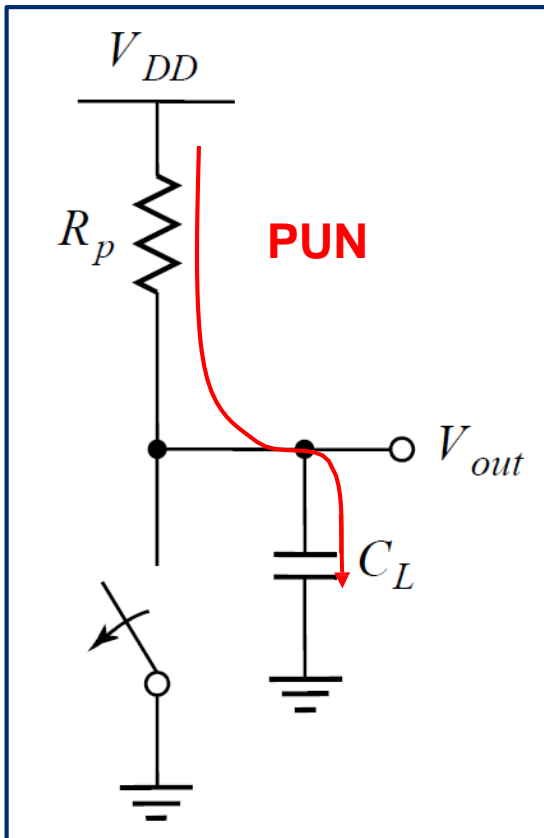

$$E_{0 \rightarrow 1}(V_{DD}) = V_{DD} \cdot C_L \cdot \int_{V_{OL}}^{V_{OH}} dV_{out} = C_L \cdot V_{DD} \cdot (V_{OH} - V_{OL})$$

□ Energy ( $V_{DD}$ ) = Energy (heat) + Energy ( $C_L$ )

$$V_{OH} = V_{DD}, V_{OL} = 0$$

$$E_{C_L} = C_L \cdot \int_{V_{OL}}^{V_{OH}} V_{out} \cdot dV_{out} = \frac{1}{2} C_L \cdot (V_{OH}^2 - V_{OL}^2)$$


$$E_{heat} = E_{0 \rightarrow 1}(V_{DD}) - E_{C_L}$$

$$E_{C_L} = E_{heat} = \frac{1}{2} C_L \cdot V_{DD}^2$$

□ During the PUN, **50% energy** dissipated in PMOS in the form of heat, the other **50% energy** stored in the  $C_L$ .
 
# Charging/discharging Consumption

$$V_{in} = V_{DD}$$
$$V_{out} = V_{DD} \rightarrow 0$$



□ Pull-Down Network:  $V_{DD}$  is disconnected!

□ Energy ( $C_L$ ) = Energy (heat)

□ The **50% energy** stored in the  $C_L$  during the previous PUN will convert to heat dissipation in NMOS for PDN.

□ Dynamic energy/power consumption **ONLY** occurs during the PUN process.

$$E_{0 \rightarrow 1}(V_{DD}) = V_{DD} \cdot C_L \cdot \int_{V_{OL}}^{V_{OH}} dV_{out} = C_L \cdot V_{DD} \cdot (V_{OH} - V_{OL})$$

# Transition Activity and Switching Power

□ Consider switching a CMOS Inverter for  $N$  clock cycles

$$E_N = C_L \cdot V_{DD}^2 \cdot n(N)$$

- $E_N$ : the energy consumed for  $N$  clock cycles
- $n(N)$ : the number of 0→1 transitions in  $N$  clock cycles

□ Average dynamic power

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f_{clk} = \left( \lim_{N \rightarrow \infty} \frac{n(N)}{N} \right) \cdot C_L \cdot V_{DD}^2 \cdot f_{clk}$$

Define activity factor

$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n(N)}{N}$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f_{clock}$$



# Switching Power of CMOS Inverter

## Capacitance:

Function of fan-out,  
wire length, transistor  
sizes  $C_{DB}$ ,  $C_W$ ,  $C_G$

## Supply Voltage:

Cannot be scaled-  
down with CMOS  
technology

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f_{clock}$$

## Activity factor:

Depend on specific  
instruction executions  
during computing

## Clock frequency:



Stop increasing since  
2005...

# Switching Power as a Function of $V_{DD}$

## Switching Power Consumption

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f_{clock}$$

## Propagation Delay

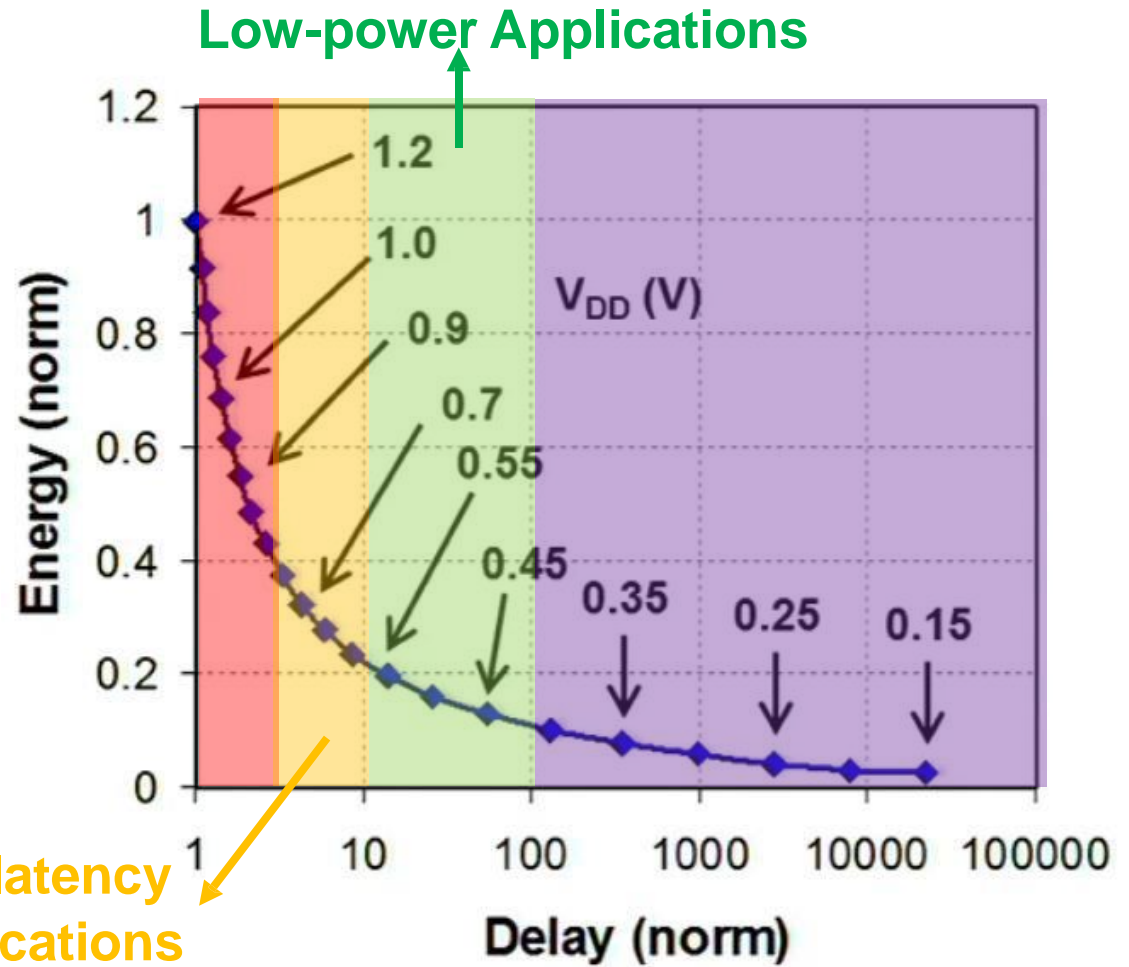 

❑ The essence of digital IC design is the compromise between power and delay!

# Dark Silicon Effect

## □ Parameters

- Switched capacitance  $C_L = 2\text{fF/gate}$  ( $V_{DD} = 1\text{V}$ ) @ 90 nm node
- Fan-out  $F = 4$
- Clock frequency  $f_{\text{clock}} = 2.5\text{ GHz}$

## □ Power per gate per switching

$$P = F \cdot C_L \cdot V_{DD}^2 \cdot f_{\text{clock}} = 4 \times 2 \times 10^{-15} \times 2.5 \times 10^9 = 20 \mu\text{W}$$

## □ Assume



- Activity factor  $\alpha = 0.1$
- $N = 1\text{ billion gates}$

$$P_{\text{tot}} = (C_L \cdot N) \cdot V_{DD}^2 \cdot (\alpha_{0 \rightarrow 1} \cdot f_{\text{clock}}) = 2000\text{ W}$$





With the power budget of 200 W, only 10% transistors can only be switched simultaneously. → **Dark Silicon Effect.**

# Short-Circuit Power Consumption

  

- In the colored region, both NMOS and PMOS are turned on, a low-impedance path formed between  $V_{DD}$  and GND → Short-Circuit Power Consumption.

# Short-Circuit Power Consumption

  

$$t_{sc} = \frac{V_{DD} - 2V_T}{V_{DD}} \cdot t_{slope} (0 \rightarrow 100\%)$$


**Triangular Approximation**

$$E_{sc} = V_{DD} \frac{I_{peak} t_{sc}}{2} + V_{DD} \frac{I_{peak} t_{sc}}{2} = t_{sc} V_{DD} I_{peak}$$


$$P_{SC} = t_{sc} \cdot V_{DD} \cdot I_{peak} \cdot f_{0 \rightarrow 1}$$
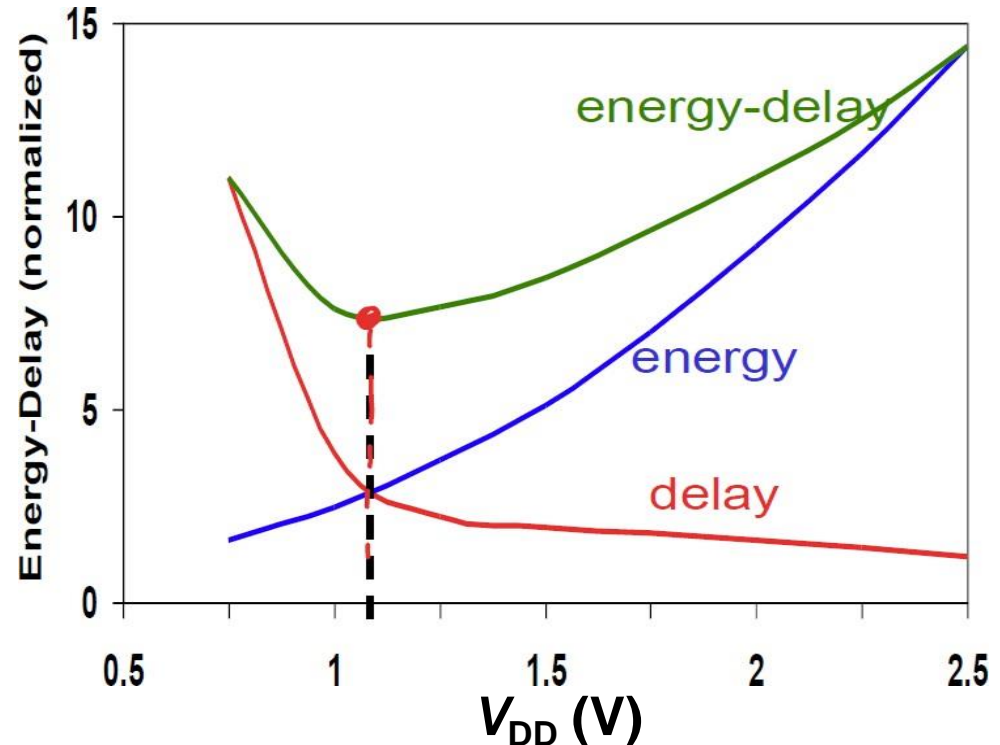
# PDP and EDP

- **Power-delay product (PDP) =  $P_{av} \times t_p = (C_L V_{DD}^2)/2$** 
  - PDP is the average energy consumed per switching event (Watts  $\times$  sec = Joule)
- **Energy-delay product (EDP)**
  - $EDP = PDP \times t_p = P_{av} \times t_p^2$
  - PDP is the average energy consumed multiplied by the computation time required.



# Summary of CMOS Inverter

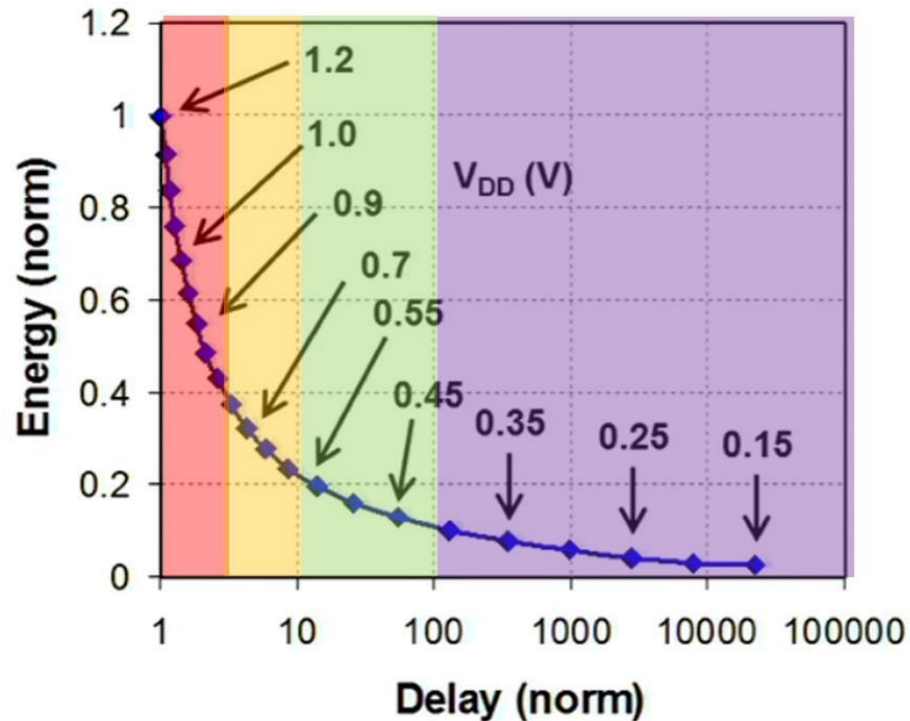

$$t_{p1} = 0.69R_0 \cdot [C_{par} + C_{g2}]$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f_{clock}$$

- The equivalent circuit of the static CMOS inverter is the **1<sup>st</sup>-order RC network**.
- Propagation delay **depend on  $V_{DD}$** , power consumption **depend on  $V_{DD}$  and gate size**.
- Smaller voltage directly reduces power consumption, yet enlarge propagation delay.
- With a  $\beta = W_p/W_n = 2$ , the **standard inverter reaches optimized condition**, and it serves as the cornerstone for the following logic circuit design.